

Enrolment No. 

--	--	--	--	--	--	--	--	--	--

**B.TECH, 3rd SEMESTER, MIDTERM EXAMINATION 2018 5, (UEC03B04) ECE**  
**NAME OF SUBJECT: ANALOG ELECTRONICS**  
**CODE NO:-UEC03B04**

Full Marks :50

Time:2 Hrs

**Answer any five (05) questions**

1. What are the reasons for variation of Operating point (Q-point) of a transistor-explain briefly. Explain how this variation is controlled in one of the Self-bias circuits. [10]
2. ~~(i)~~ Derive the simplified expression of voltage gain for a small signal CE amplifier using h-parameter or r-parameter model.  
(ii) What is the problem of cascading CE and CB amplifier? How this problem may be overcome? (6+4 = 10)
3. ~~(i)~~ Classify power Amplifier in terms of conduction angle. For Push-Pull Class B Amplifier determine the overall efficiency of the Amplifier.  
(ii) For a class B amplifier (Push-Pull type) providing a 25 V peak signal to a 20  $\Omega$  load (speaker) and a power supply of VCC = 30 V, determine the input power, Output power and Circuit Efficiency. (5+5=10)
4. A Class A transformer coupled Amplifier is designed to deliver a maximum 5.5W power to a 4 $\Omega$  load. Operating point is adjusted for symmetrical clipping with collector supply voltage of 20V. Assume ideal characteristic with  $V_{min} = 0V$ . Calculate,  
(i) Transformer turns ratio, (ii) Peak collector current, (iii) Operating current ( $I_{ceq}$ ) and voltage ( $V_{ceq}$ ),  
(iv) Collector circuit efficiency and (v) Power dissipation rating of the transistor. [10]
5. How non-linear and Cross-over distortion is removed in class B power Amplifier? [10]
6. (i) Why there is lower cut-off frequency in RC-coupled Amplifier?  
(ii) For voltage series negative feedback circuit configuration determine the input impedance and output impedance. Let, without feedback input impedance, output impedance and voltage gain are  $Z_{in}$ ,  $Z_{out}$  and A respectively. Gain of the feedback circuit is B. [2 + 8 = 10]